

VCXO Application Guideline for CDCE(L)9xx Family

Ivo Marocco
High Speed - Clock Drivers

ABSTRACT

This application report focuses on the VCXO application, explaining the characteristics that the crystal unit must have to meet the device specifications, giving advice on package and assembly to reduce the impact of unwanted effects and concluding with a list of recommended crystals.

Contents

1	Introduction	1
2	CDCE(L)9xx VCXO On-Chip Implementation	2
	2.1 Architecture Overview	2
	2.2 Quartz Crystal: General Theory and Basics Equations	2
3	CDCE(L)9xx Crystal Specifications	4
	3.1 Requirements	4
	3.2 Load Capacitance	4
	3.3 Absolute Pulling Range	6
	3.4 Crystal Specification for Non-VCXO Application	6
4	Layout Considerations	6
5	Recommended Crystals	7
6	References	7

List of Figures

1	CDCE(L)9xx VCXO Architecture	2
2	Crystal Equivalent Circuit	2
3	Crystal Impedance Characteristic	3
4	Pullability Characteristic Versus Control Voltage	4
5	Varicap Characteristic Versus Control Voltage	5
6	Load Capacitance Characteristic	5
7	Pulling Range Curves Comparison	7

List of Tables

1	List of Recommended Crystals for VCXO Application	7
---	---	---

1 Introduction

The CDCE(L)9xx programmable clock generator offers the possibility for the input to be driven either by an LVCMOS clock signal or by a crystal unit.

Because the device has an on-chip integrated VCXO, the output frequency produced can be tuned by means of an analog input voltage, allowing the synchronization of the output signal with the input (i.e., a PWM signal).

2 CDCE(L)9xx VCXO On-Chip Implementation

2.1 Architecture Overview

The external crystal unit is attached to the device in order to build a parallel resonant oscillator as depicted in [Figure 1](#).

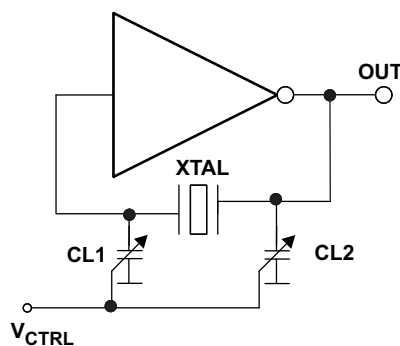


Figure 1. CDCE(L)9xx VCXO Architecture

This kind of architecture provides a feedback path through the crystal unit and the load capacitors. Changing the analog control voltage that acts on these capacitors (also called varactors) allows the adjustment of the output frequency. The latter is thus defined by the programmable CL1, CL2 (that are on-chip integrated), and by the crystal unit.

2.2 Quartz Crystal: General Theory and Basics Equations

The electrical properties of the crystal unit can be represented by the equivalent circuit depicted in [Figure 2](#).

 


Figure 2. Crystal Equivalent Circuit

R1 is the equivalent series resistor (resistive losses), L1 is the motional inductance (oscillating mass), C1 is the motional capacity (elasticity of the oscillating body), and C0 is the shunt capacity (static parallel capacitor). C1 depends on the electrode area and can be changed by changing the cut of the crystal, whereas C0 is the capacity between the vacuum-deposited metal electrodes and the quartz material as a dielectric. By neglecting the resistive losses, the impedance of a quartz crystal can be considered as a pure reactance whose expression is given as the relationship between the voltage difference applied at its terminals and the current flowing and whose behavior over the frequency range can be seen in [Figure 3](#).

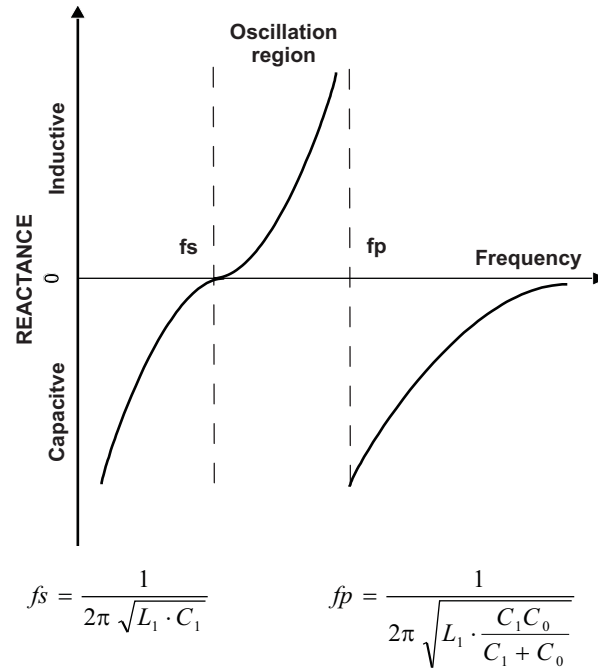


Figure 3. Crystal Impedance Characteristic

The reactance phase is 0 at two frequencies; the first is the series resonant frequency (f_s) and the second is the parallel resonant frequency (f_p). The frequency region between f_s and f_p is the oscillation region and the wider this region is, the more pullable the crystal is. The pullability coefficient for any crystal is calculated from the relationship between the shunt capacity and the motional capacity $p = C_0/C_1$.

Mathematically f_s and f_p are linked as follows:

$$f_p = f_s \times \sqrt{1 + \frac{C_1}{C_0}} \rightarrow f_s \times \sqrt{1 + \frac{1}{p}} \quad (1)$$

It is clear that the smaller the pulling coefficient p is, the larger the distance of f_p from f_s is. Considering the circuit in [Figure 1](#), the effect of the capacitive load is the shifting of the operative frequency of a certain offset over the f_s . The operative frequency f_l (load) is calculated as follows:

$$f_l = f_s + f_s \times \frac{C_1}{2 \times (C_0 + C_L)} \quad (2)$$

The offset due to the load capacity also can be written as follows:

$$\frac{f_l - f_s}{f_s} = \frac{C_1}{2 \times (C_0 + C_L)} \quad (3)$$

The variation of the offset with the load capacity is another important parameter for a crystal called sensitivity, defined as:

$$S = \frac{\delta_{\text{offset}}}{\delta_{C_L}} = \frac{C_1}{2 \times (C_0 + C_L)^2} \quad (4)$$

3 CDCE(L)9xx Crystal Specifications

3.1 Requirements

So far, some important parameters and mathematical equations of a quartz crystal have been discussed in general. How do these relate to the CDCE(L)9xx requirements? Looking at the 27-MHz video applications for which the device can be used for synchronization purposes, the most important specification of the VCXO is the pulling range. This is the frequency range in which the operative frequency can be swept by sweeping the control voltage. Typical values have an order of magnitude of some ppm (part per million) of the center frequency. The CDCE(L)9xx specifies a typical value of 120 ppm over a voltage that ranges from 0 V to 1.8 V (see Figure 4).

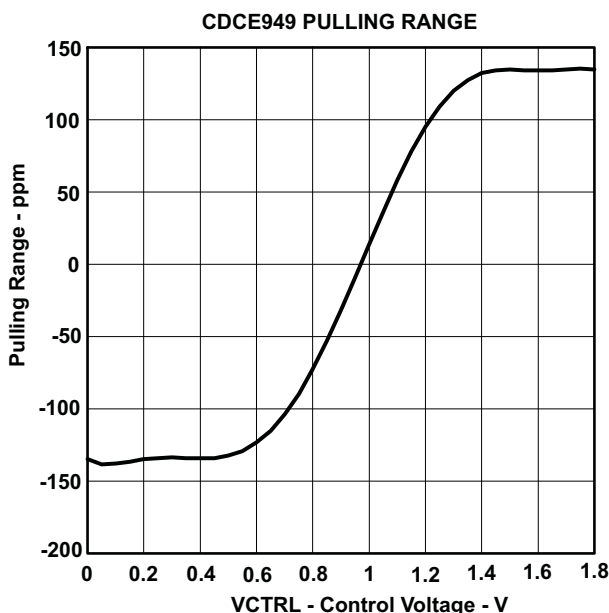


Figure 4. Pullability Characteristic Versus Control Voltage

For the crystals (used for the VCXO application) to fulfill this requirement the ratio $p = C0/C1$ should be close to 220 (or even smaller). Having $C1 > 20$ pF also ensures better performances (pullability > 120 ppm).

The ESR should be as small as possible to ensure the start-up, and the $C0$ must be smaller than 6 pF. A larger value could have an impact on the start-up capability of the VCXO.

3.2 Load Capacitance

The load capacitance is, per definition, the value of capacitance measured, or calculated, across the connection points of the crystal. That is, it takes into account not only $CL1$ and $CL2$ but also the stray capacitance Cs (capacity of the crystal socket plus any other parasitic from both PCB and chip across the crystal).

$$C_L = CL_{On-Chip} + Cs \rightarrow CL_{On-Chip} = \frac{CL_1 \times CL_2}{CL_1 + CL_2} \tag{5}$$

$CL_{On-Chip}$ is the on-chip programmable capacitance, also called varactor. The CDCE(L)9xx offers the opportunity to program it from 0 pF up to 20 pF with 1-pF steps, by changing the bit [7:3] of the register 05h (see data sheet [SCAS844](#)). The default value is 10 pF.

By knowing the total load capacitance CL from the crystal specification and Cs from the data sheet, it is possible to calculate the value of $CL_{On-Chip}$ by subtraction and program it selecting the appropriate bit configuration.

Once $CL_{\text{On-Chip}}$ has been set to the desired value, the variation of the control voltage in the range between 0 V and 1.8 V allows a corresponding sweep of the varactor's value from $1.3 \times CL_{\text{On-Chip}}$ (30% higher than starting value) up to $0.3 \times CL_{\text{On-Chip}}$ (70% lower than starting value). For further clarification, see the curve appearing in [Figure 5](#).

 


Figure 5. Varicap Characteristic Versus Control Voltage

Whether the pulling range requirement is met depends on the sensitivity that the chosen crystal has for that load $CL_{\text{On-Chip}}$. The control voltage has an effect on the $CL_{\text{On-Chip}}$ only and not on the parasitic, making it clear why is important to reduce them. A high parasitic causes a reduction of pulling range.

[Figure 6](#) shows an example of frequency variation versus load capacitance, also called load capacitance characteristic, for a given crystal that has a trim sensitivity of 25 ppm/pF for a load capacitance of 12 pF.

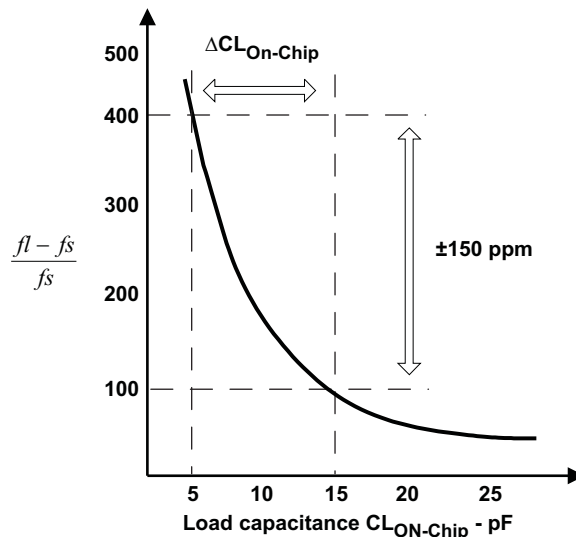


Figure 6. Load Capacitance Characteristic

In the upper example of [Figure 6](#), a variation of the control voltage is translated in a variation of the varactor value from its center target value (12 pF) to the corners (3.6 pF and 15.6 pF), for a total delta of 12 pF. Such a change has the effect to make the output frequency drift, giving a final pulling range of $(12 \text{ pF} \times 25 \text{ ppm/pF})$ approximately 300 ppm ($\pm 150 \text{ ppm}$).

3.3 Absolute Pulling Range

The VCXO also can be considered as a resonator that locks to its reference (the kick-off) that is the quartz crystal. The VCXO-crystal system is affected from inaccuracy due to temperature stability, aging, circuit variation, and so on. The absolute pulling range is what is left from the nominal pulling range after subtracting all the error contributions. This parameter is an indication of how good the VCXO can follow the crystal and lock to its fundamental mode.

Referring once again to the previous example (± 150 ppm) and considering the following error contributions:

Frequency tolerance	20 ppm
Temperature stability	30 ppm
Aging	15 ppm
Circuit variation	15 ppm

the absolute pulling range is ± 70 ppm.

3.4 Crystal Specification for Non-VCXO Application

When the VCXO is not employed and the device is driven from a crystal, its requirements are much more relaxed, as a pulling range is unnecessary.

The quartz crystal fundamental frequency ranges from a minimum of 8 MHz up to a maximum of 32 MHz. The requirements for the electrical specification of these crystals concern the equivalent series resistors (ESR) and the shunt capacity (C0).

The first must be smaller than 100 Ω , whereas the latter must be smaller than 6 pF to ensure start-up conditions.

4 Layout Considerations

As previously mentioned, any parasitic across the crystal reduces the pullability of the VCXO. Therefore, care must be taken in placing the crystal units on the board. Always place it as close to the device as possible, ensuring that the routing lines from the crystal terminals to XIN and XOUT have the same length. If possible, cut out both ground plane and power plane under the area where the crystal and the routing to the device are placed. In this area, always avoid routing any other signal line, as it could be a source of noise coupling.

Additional discrete capacitors can be required to meet the load capacitance specification of a certain crystal. For example, a 10.7-pF load capacitor is not fully programmable on the chip, because this can range from 0 pF to 20 pF with steps of 1 pF.

The 0.7-pF capacitor therefore can be discretely added. In order to minimize the inductive influence of the trace, it is recommended to place this small capacitor as close to the device as possible and symmetrically with respect to XIN and XOUT.

5 Recommended Crystals

Table 1 provides a list of crystals that meet the device requirements.

Table 1. List of Recommended Crystals for VCXO Application

Crystal Manufacturer	Part Number
KDS	SMD-49
KDS	DSX530GA
KVG	XA 3648
NewXtal	C18P06002 SMD 5032
Pletronics	SMT13T065
Quartzcom	UM-1 MJ

The pullability of the VCXO for a given crystal, by just inserting its electrical specifications (C0, C1, CL, and L1), can be simulated. TI Pro-Clock™ programming software (available on the TI Web site for the CDCE9xx) offers this feature. Figure 7 shows the comparison between the pullability curve calculated with the platform and that measured in the laboratory.

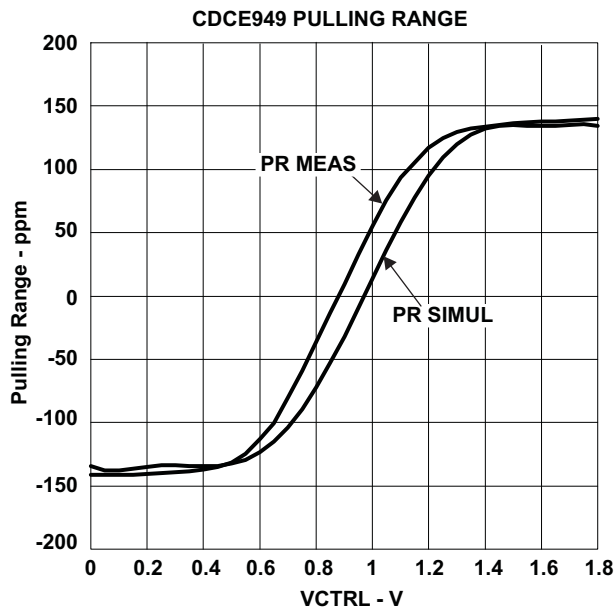


Figure 7. Pulling Range Curves Comparison

6 References

- Schwingquarze: ein unverzichtbares Bauelement in der Elektronik (Vistas Verlag, Berlin)
- *High-Speed Layout Guidelines* application report ([SCAA082](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
Low Power Wireless	www.ti.com/lpw	Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated