

## MAKE A PRECISION -10V REFERENCE

By R. Mark Stitt (520) 746-7445

The need for a precision -10.0V reference arises often. For example, the best way to get a 0V to +10V output from a CMOS MDAC is to use a -10V reference (see Figures 4-6). ADI/PMI has the REF-08 -10V reference, but it has limited performance. Although Burr-Brown offers no -10V reference, the REF102 precision +10.0V reference can be accurately converted to a precision -10.0V reference. The circuit is simple and requires no precision components. The 2.5ppm/°C temperature drift of the Burr-Brown REF102 is twenty times better than the 50ppm/°C best grade of the PMI REF-08. (Even our lowest grade is five times better.)

The simplest approach for converting a REF102 into a -10.0V reference is shown in Figure 1. The only extra component is a 1kΩ resistor connected to -V<sub>S</sub>. This circuit is useful, but has limitations. Maximum expected load current plus maximum reference quiescent current must be supplied by the resistor at minimum -V<sub>S</sub>. Changes in current resulting from load and power supply variations must be driven by the reference. The excess current through the reference reduces its accuracy due to drift from self-heating and thermal feedback. Changes in reference output current due to power-supply variations translate into line regulation error. Voltage reference load regulation is not usually as good as line regulation. Finally, the output impedance due to the resistor pull-down causes settling problems with dynamic loads.

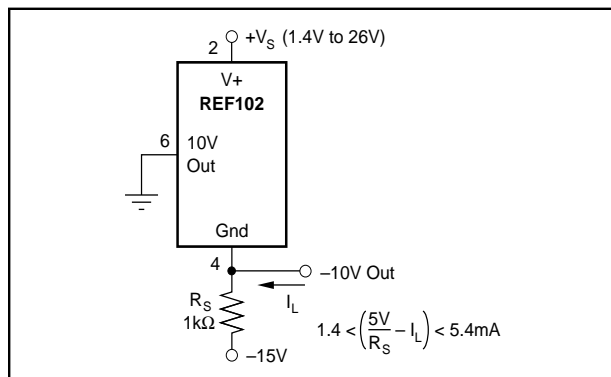


FIGURE 1. Simple -10V Reference.

The circuit shown in Figure 2 solves these problems. As in Figure 1, no precision resistors are needed. The error contributed by the op amp is negligible (the OPA27 0.6μV/°C V<sub>OS</sub>/dT adds only 0.06 ppm/°C drift to the -10V reference). As a bonus, the circuit incorporates noise filtering.

 


FIGURE 2. Improved -10V Reference.

To understand how the circuit works, notice that the reference is in the feedback loop of the op amp. The op amp output forces the Gnd connection of the reference to exactly -10.0V so that the voltage at the op amp inverting input is the same as at its noninverting input (ground). Since no current flows into the op amp input, the reference output current remains at zero, eliminating voltage reference thermal feedback or load regulation errors. The R<sub>1</sub>, C<sub>1</sub> network assures loop stability and provides noise filtering. Reference noise is filtered by a single pole of  $f_{-3dB} = 1/(2 \cdot \pi \cdot R_1 \cdot C_1)$ . Bias current flowing through R<sub>1</sub> can produce DC errors and noise. If a lower filter pole is needed, keep R<sub>1</sub> = 2kΩ and increase C<sub>1</sub> to preserve accuracy.

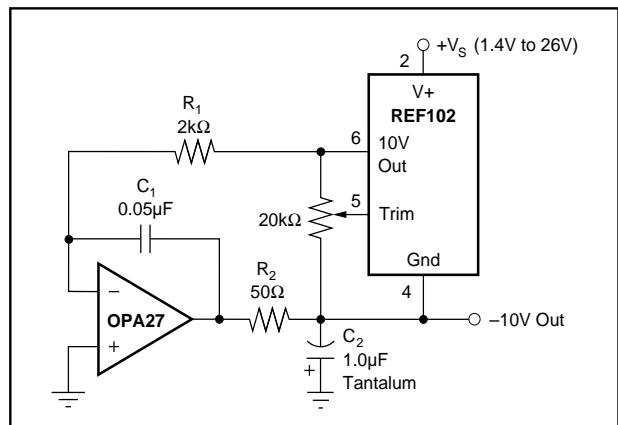


FIGURE 3. Improved -10V Reference with Improved Filter, with V<sub>OUT</sub> Trim.

 


FIGURE 4. Precision 0V to +10V Output DAC.

Figure 3 shows an improved filter and a provision for output voltage adjustment. The 20kΩ pot can be used for fine adjustments or to increase the output to -10.24V for 10mV per 10-bit LSB—ideal in many binary DAC applications. The improved filter:

1. Provides low output impedance at high frequency for driving dynamic loads,
2. Improves noise filtering, and
3. Drives large capacitive loads—see AB-003.

Figure 4 shows the preferred way to connect a CMOS MDAC for a 0 to +10V output. This approach is less expensive and provides better accuracy than the other approaches shown below.

The circuit shown in Figure 5 is commonly used to get a 0 to +10V output with a CMOS MDAC. The disadvantage with this circuit is that it requires an extra op amp and pair of precision resistors for each DAC. Also, settling time increases because two amplifiers must settle in the signal path. For good settling time, both amplifiers must be fast settling. Then settling time increases by the square-root-of-the-sum-of-the-squares of settling time for each amplifier.

The circuit shown in Figure 6 can also be used to get a 0 to +10V output from a CMOS MDAC. The problem with this circuit is nonlinearity due to code-dependent voltage across the switches within the DAC. Using a 2.5V reference and gain at the output, as shown, mitigates this error, but you still need a pair of precision resistors for each DAC. The appropriate use for this circuit is in +5V single-supply applications. With a 2.5V reference and a unity-gain, single-supply buffer, the output will be 0 to +2.5V.

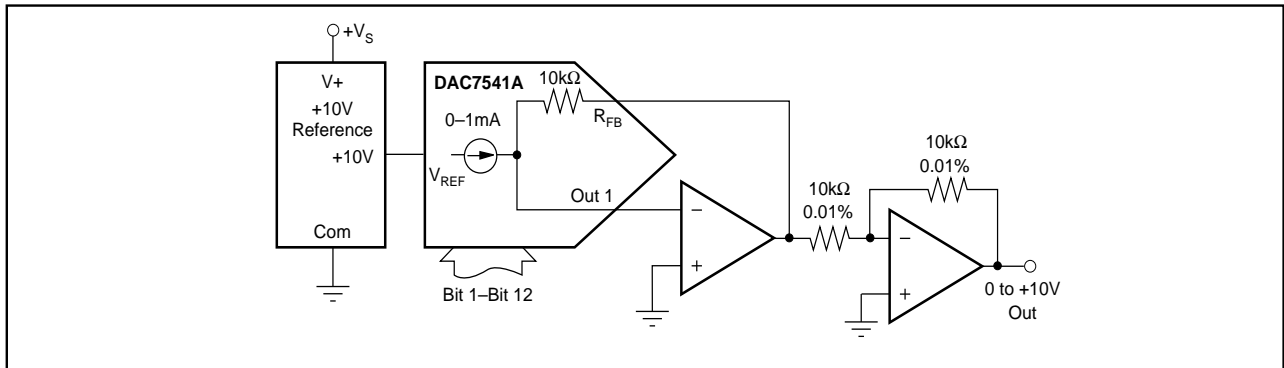


FIGURE 5. Another 0V to +10V Output DAC.

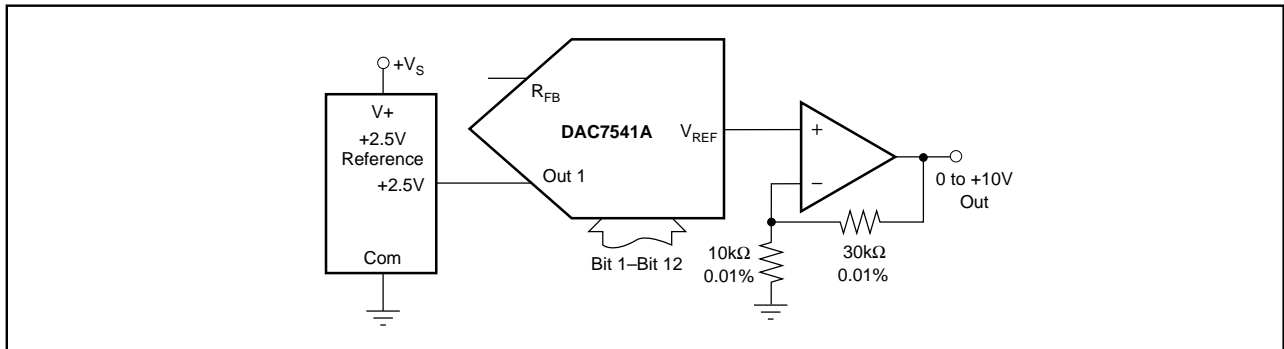


FIGURE 6. Single Supply 0V to +10V.

The information provided herein is believed to be reliable; however, BURR-BROWN assumes no responsibility for inaccuracies or omissions. BURR-BROWN assumes no responsibility for the use of this information, and all use of such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. BURR-BROWN does not authorize or warrant any BURR-BROWN product for use in life support devices and/or systems.

## **IMPORTANT NOTICE**

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.